




PSPICE  
(2. Transient Analysis)  
for  
Network Analysis & Lab

Dr. Charles J. Kim

Howard University
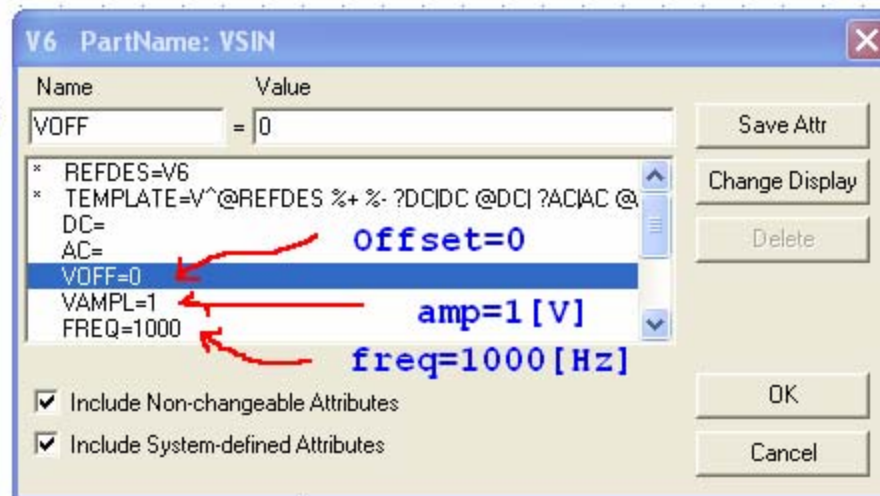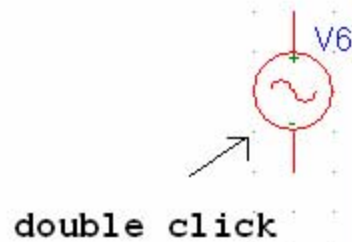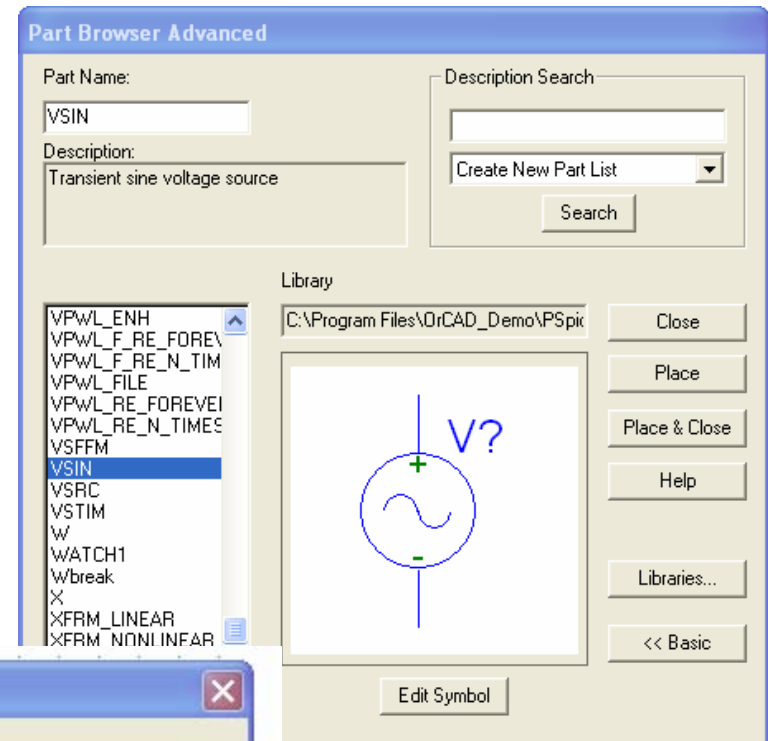
# Sinusoidal Source: VSIN

- Sinusoidal source placement:  
**VSIN**
- Amplitude and Frequency Setting
- Don't forget to set  $V_{OFF}=0$



# Triangular Source: VPULSE


**Part Browser Advanced**

Part Name:


Description:

Description Search:

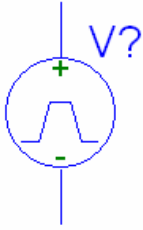Library: C:\Program Files\OrCAD\_Demo\PSpic




Vpulse

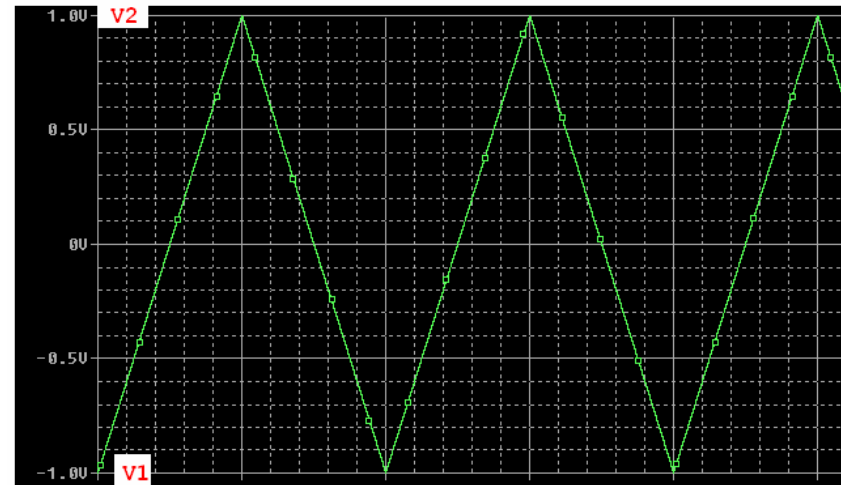

For Amp=1 and Freq=1000Hz case

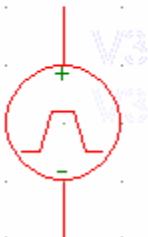V1 : lowest value    V1 = -1  
 V2 : highest value    V2 = 1  
 Tr : rising time    Tr = 0.5ms  
 Tf : falling tim    Tf = 0.5ms  
 Pw : Pulse width    Pw = 1us (actually 0)  
 Per: Period    Per= 1ms






**V3 PartName: VPULSE**

Name	Value
PER	= 1ms
V1=-1	
V2=1	
TD=	
TR=0.5ms	
TF=0.5ms	
PW=1u	
PER=1ms	

Include Non-changeable Attributes  
 Include System-defined Attributes

# Square Source: VPULSE

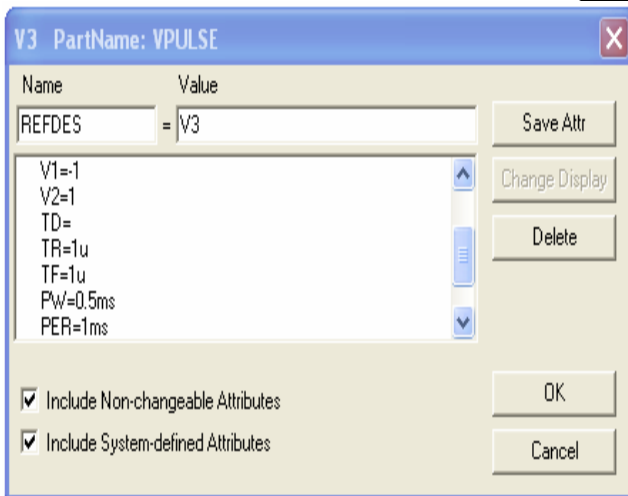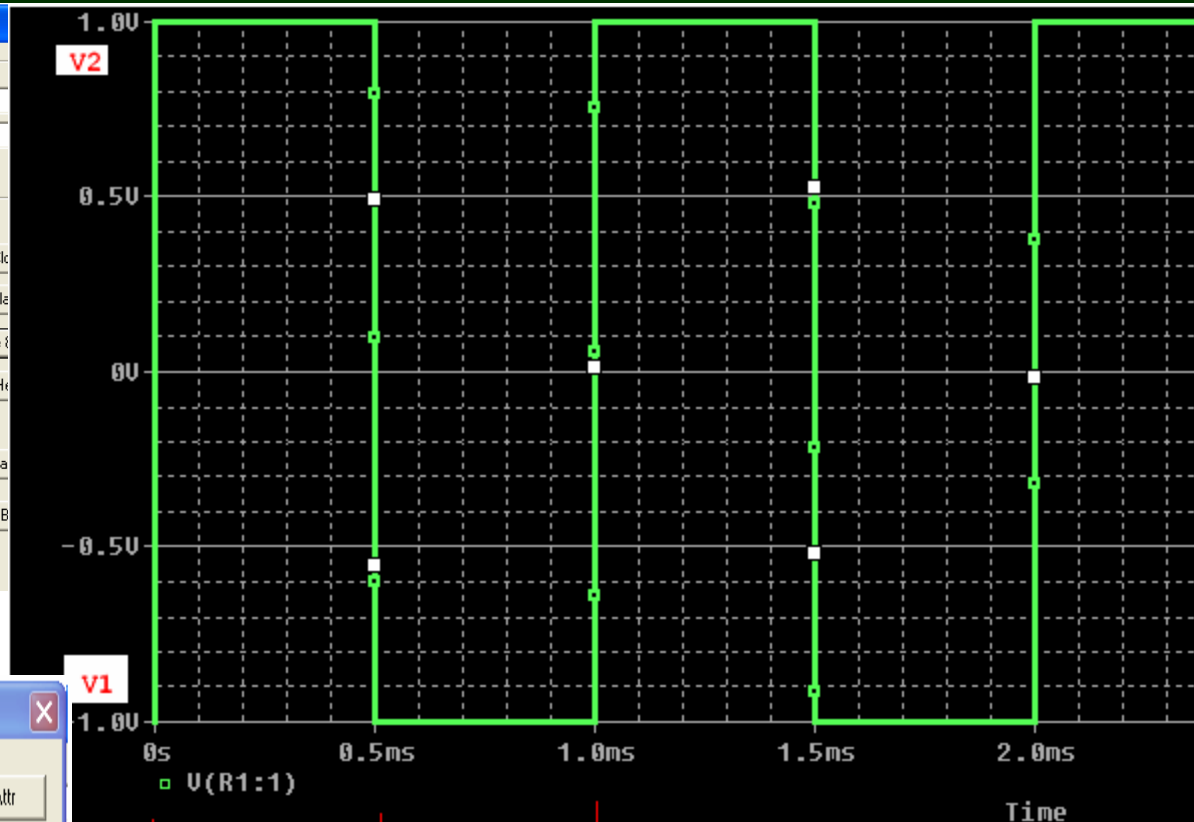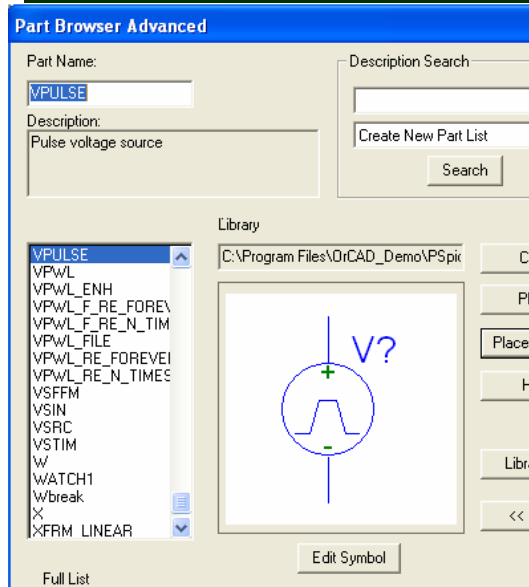


V1 : lowest value  
V2 : highest value  
Tr : rising time  
Tf : falling time  
Pw : Pulse width  
Per: Period

For AMp=1 and  
Freq=1000Hz case




V1 = -1  
V2 = 1  
Tr = 1u (actually 0)  
Tf = 1u (actually 0)  
Pw = 0.5 ms  
Per= 1 ms

# RC Circuit Example


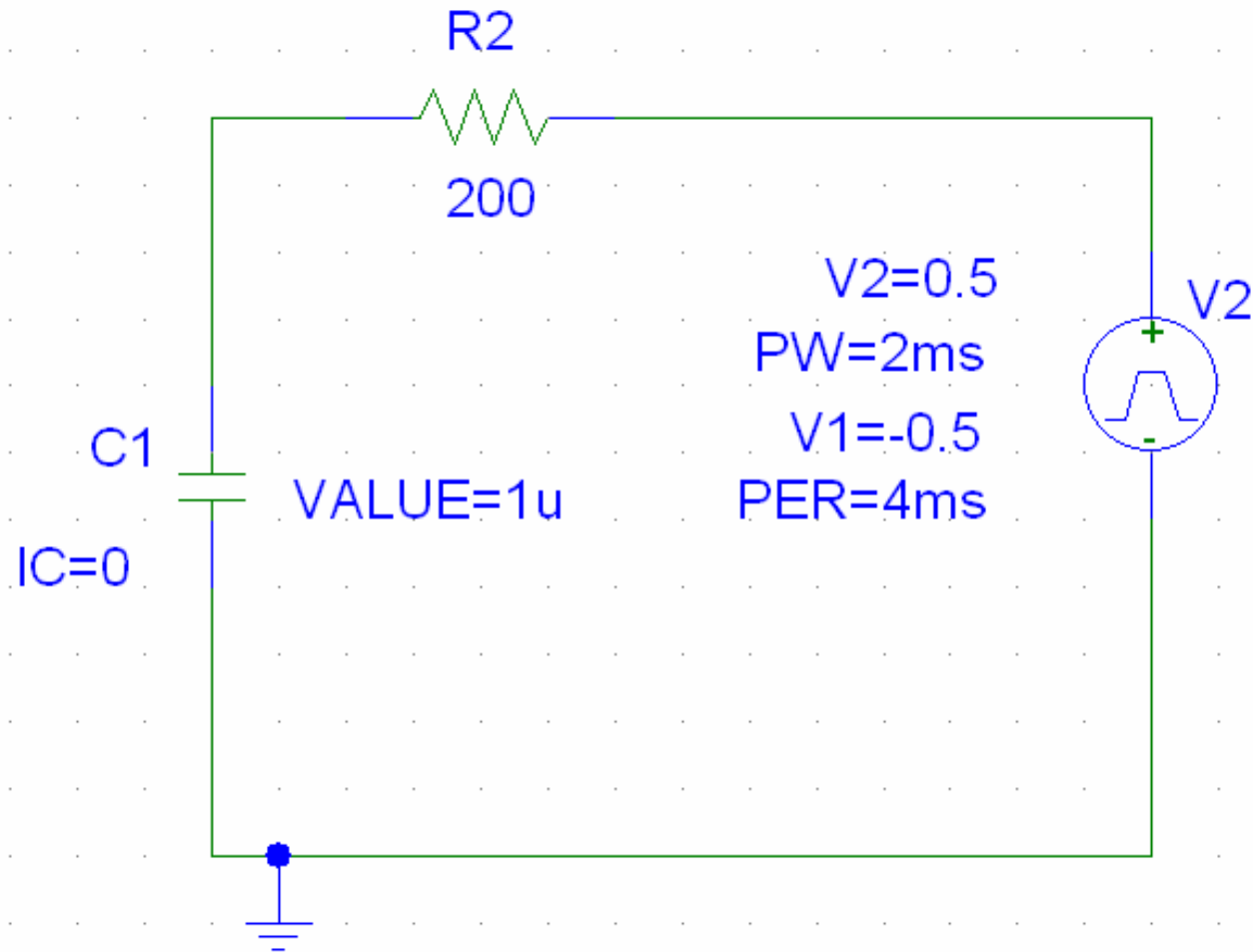

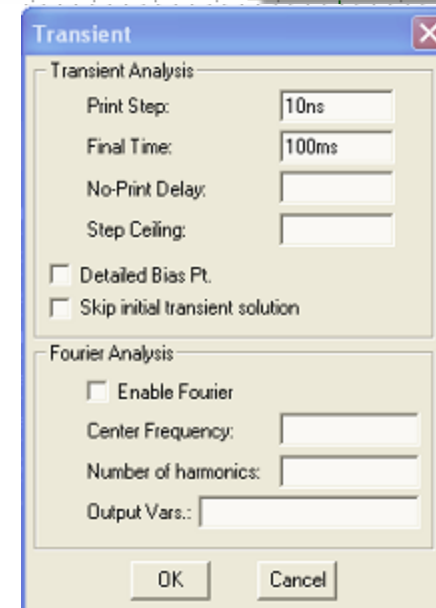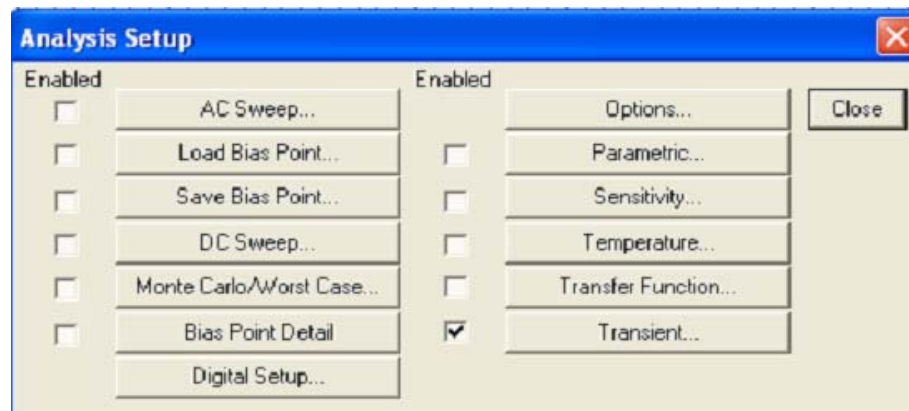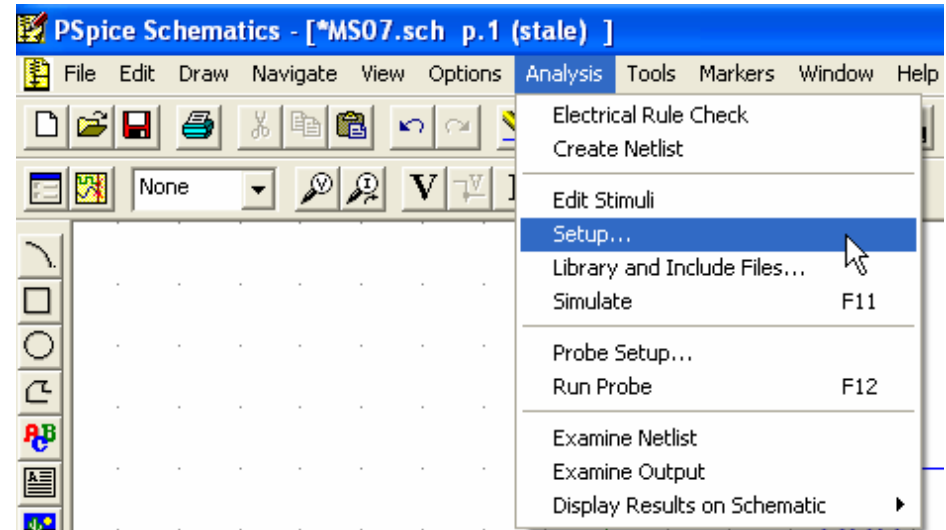
# Transient Analysis: Set up


- Menu > Analysis > Setup
- Click on the Transient tab
- Print Step
- Final Time




# Transient Analysis: V & I Markers

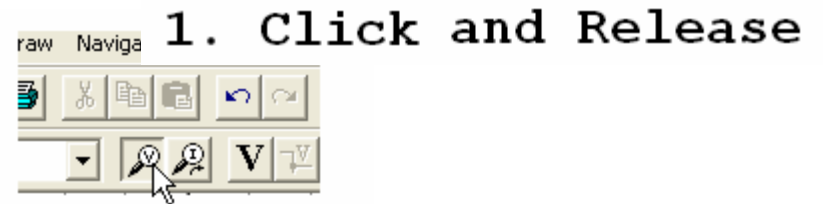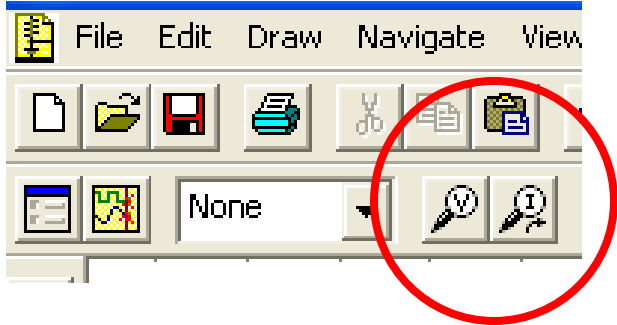

2. Drag it

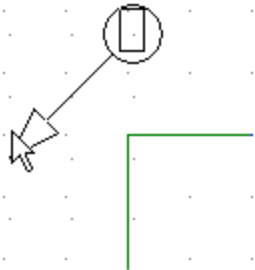

3. Place it

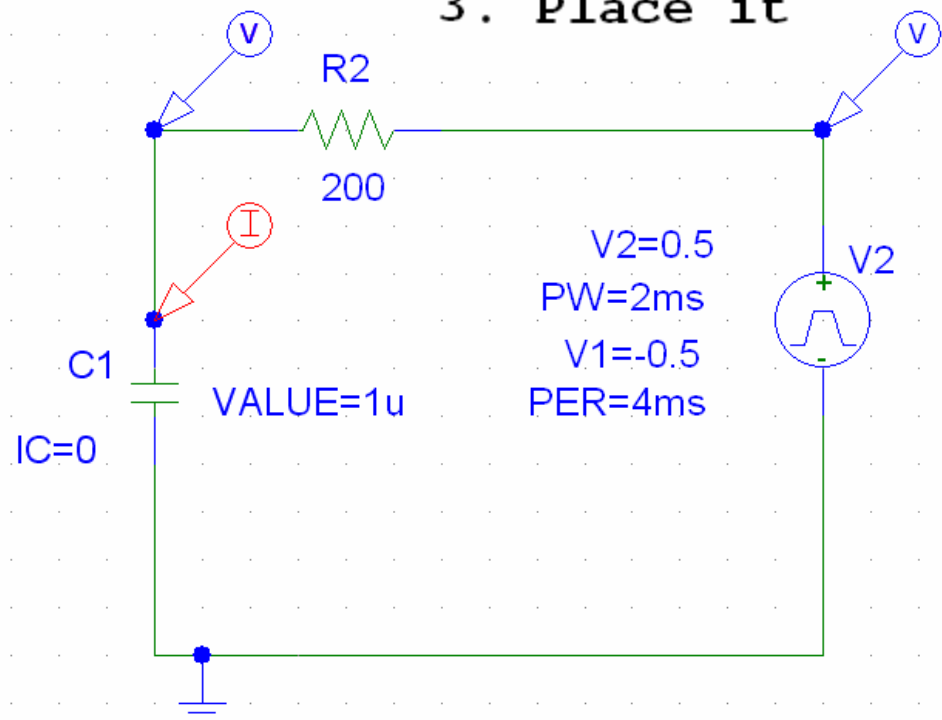

# Simulate it

