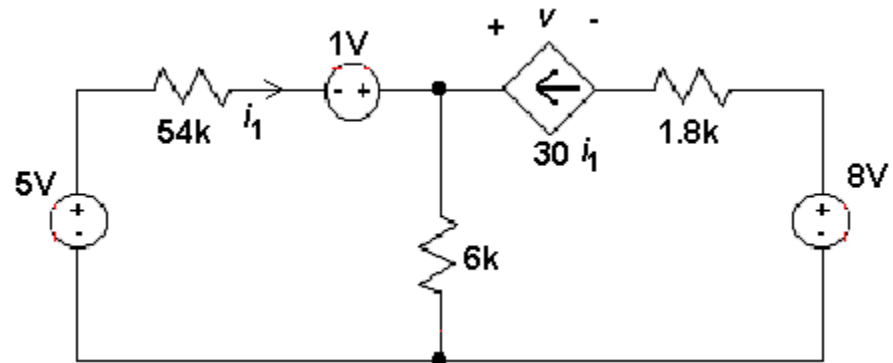


Class Note 3: Example Problem with Dependent Source

Problem 1:


Find v and i_1 from the circuit given below



SOLUTION:

Strategy: KCL at the center node for current calculation, and KVL for the voltage.

(a) node and current marks and loops

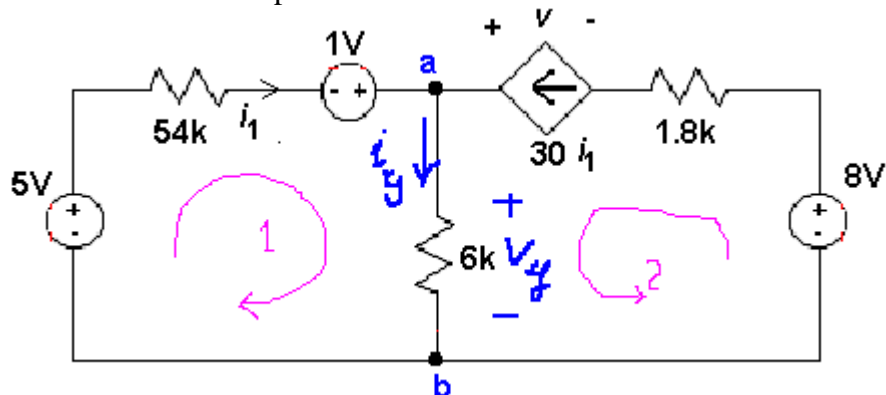


(b) Equations:

Problem 2:

In a given circuit below, all the resistances and sources are known: $V_{cc}=15[V]$, $V_o=200[mV]$, $R_1=20K$, $R_2=80K$, $R_E=100$, and $R_C=500$. $\beta=39$.

Find equation for i_B and I_{cc} .

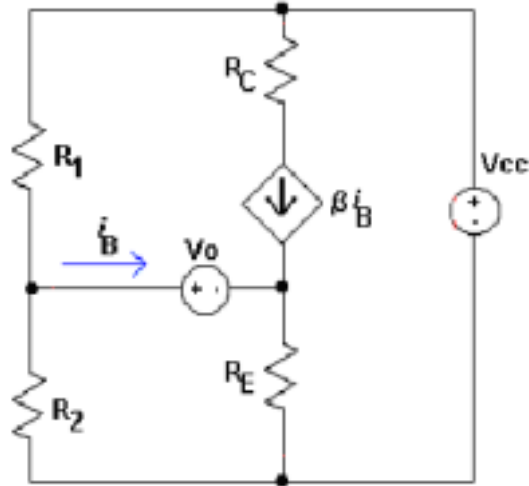

SOLUTION

Procedure:

1. The first thing we do is to mark nodes (a, b, c, and d) and flow indication of the currents (i_1 , i_2 , i_B , i_E , i_C , and i_{cc})

