

Class Note 07: $\Delta \leftrightarrow Y$ Transformation Example

Problem Setting:

Find currents i_0 , i_1 , and i_2 of the circuit below.

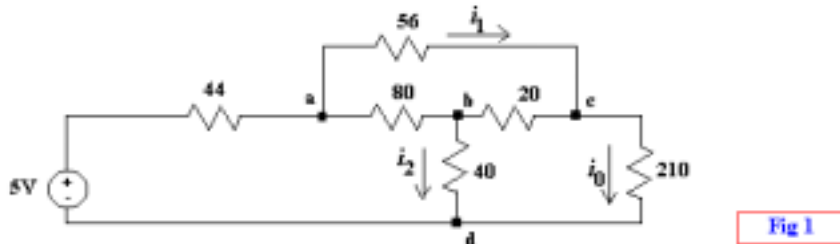


Fig 1

SOLUTION

1. Let's observe the circuit before we make any move. Do you see Y and Δ resistors?

Yes, we see them as shown below. But remember, in most of circuit problems, it's an one way traffic as far as the transformation direction concerns: $\Delta \rightarrow Y$.

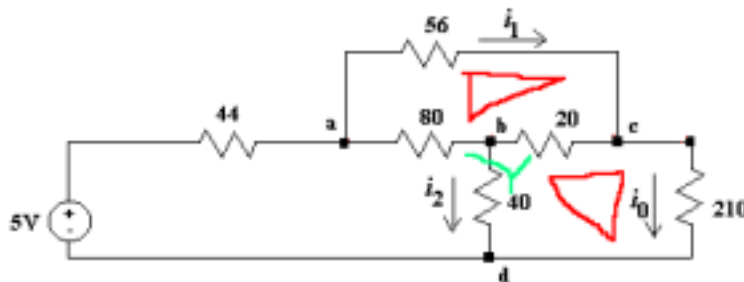


Fig 2

2. If you convert the Δ resistors (right side) to Y then it looks like this: *Why not the top Δ ?*

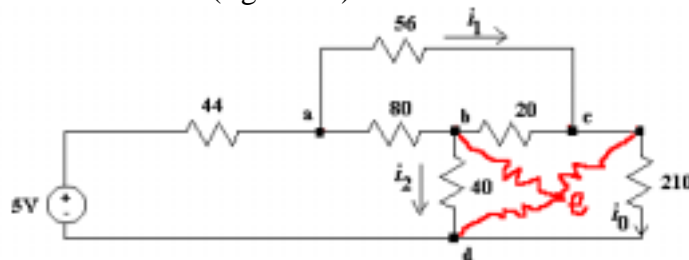


Fig 3

Here we have to remember that: $i_2 = \frac{V_{bd}}{40}$ and $i_0 = \frac{V_{cd}}{210}$; i_1 is the current through 56Ω resistor

3. Now we have the following simplified circuit:

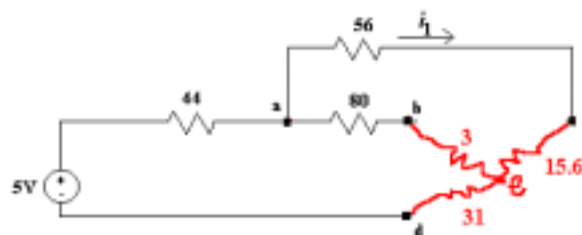


Fig 4

4. It further simplifies to:

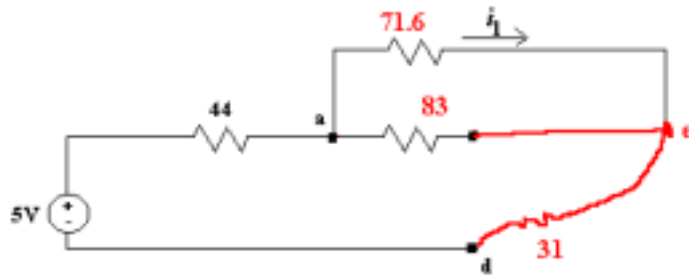


Fig 5

4. Finally, the circuit is reduced to a single loop one:

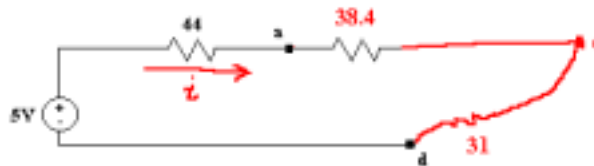


Fig 6

5. Then the current flowing through the resistors is: $i = \frac{5}{(44 + 38.4 + 31)} = 0.044 \text{ [A]}$ (Fig.6)

6. Now let's find currents by the following steps: (it looks like a wave propagation, or, stating from an open cell, marking mines or opening neighboring cells, in your famous minesweeper game. Or do you feel it?)

(1) The voltage $V_{ae} = 0.044 \times 38.4 = 1.69 \text{ [V]}$ (Fig.6)

(2) Therefore the current $i_1 = \frac{V_{ae}}{71.6} = 0.0236 \text{ [A]}$ (Fig.5)

(3) The current through the 80 resistor is: $i_{80} = \frac{V_{ae}}{83} = 0.02036 \text{ [A]}$ (Fig. 4)

(4) Therefore, voltage $V_{ab} = i_{80} \times 80 = 1.63 \text{ [V]}$ (Fig.4 and Fig.3)

(5) Also, voltage $V_{ad} = i \times (38.4 + 31) = (0.044)(69.4) = 3.0536 \text{ [V]}$ (Fig. 6)

(6) Then, from above two voltages, we have voltage:

$$V_{bd} = V_{ad} - V_{ab} = 3.0536 - 1.63 = 1.4236 \text{ [V]} \text{ (Fig. 3)}$$

(7) Then, current $i_2 = \frac{V_{bd}}{40} = \frac{1.4236}{40} = 0.0356 \text{ [A]}$ (Fig. 3)

(8) By KCL at node b , we get the current through 20 resistor (toward right):

$$i_{20} = i_{80} - i_2 = -0.01524 \text{ [A]} \text{ (Fig. 2)}$$

(9) Therefore, $i_0 = i_1 + i_{20} = 0.0236 + (-0.01524) = 0.00836 \text{ [A]}$ (Fig. 2)