

**Class Note 16:****Node-Voltage Method vs. Mesh-Current Method - which is better and when?****General (meaning "not always true") selection rule:**

Pick one which results in fewer equations by comparing the number of:

- (a) unknown node voltages and
- (b) unknown mesh currents.


**Adage**

"Some time spent thinking about the circuit analysis problem in relation to the various approaches (node and mesh included) is time well spent."

**CASE 1:**

The question with the circuit below is to find the power dissipated in the  $10\ \Omega$  resistor. Which method, node or mesh, do you want to pick?

Let's apply the general rule to select a better approach.

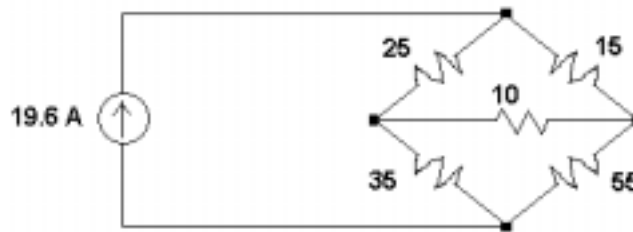**SOLUTION**

(1) Strategy? : Find the current through the  $10\ \Omega$  resistor ( $i_{10}$ ) since  $P_{10} = (i_{10})^2(10)$ .

(2) Nodes: 3 + reference


Meshes: 3 but (one is already known with 19.6)

(3) Verdict: Mesh-Current Method.

Let's mark the mesh currents as follows.

See that the mesh current  $i_c$  is the same as the source current, 19.6.

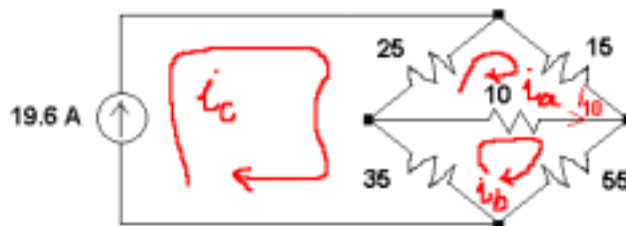Also,  $i_{10}$  now is:  $i_{10} = i_b - i_a$



(4) Calculation.

$$\text{@ Mesh a: } 25(i_a - 19.6) + 15i_a + 10(i_a - i_b) = 0 \quad \text{-----} > \quad 5i_a - i_b = 49 \quad \text{-----} (1)$$


$$\text{@ Mesh b: } 35(i_b - 19.6) + 10(i_b - i_a) + 55i_b = 0 \quad \text{-----} > \quad -10i_a + 100i_b = 686 \quad \text{-----} (2)$$

By (1)\*2 + (2):  $98i_b = 784$ , therefore,  $i_b = 8$  and  $i_a = 11.4$

Then  $i_{10} = i_b - i_a = -3.4$ .

Finally,  $P_{10} = (i_{10})^2(10) = 115.6\ \text{[W]}$ .

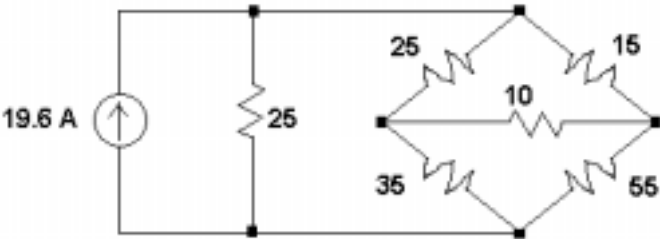CASE 2: From the case 1, we inserted a  $25\Omega$  resistor and the question again is to find the power dissipated in the  $10\Omega$  resistor. What method are you going to apply?



**SOLUTION:**

Nodes: 3 + Reference (3 variables)  
 Meshes:  $4-1=3$  (3 variables).  
 Verdict: ?????

