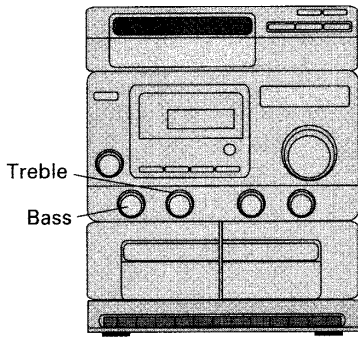


Note09: Active Filters ---Part 3: Practical Perspectives

Note; This discussion is essential to your success in the project

6. Practical Perspective (Bass Volume Control)




1. Objective


- (i) OP Amp Circuit
- (ii) Amplification of an audio signal in the bass range
- (iii) audio signal range: 20 - 20000 Hz
- (iv) bass range: 20 - 300 Hz
- (v) Bass Volume Control Circuit Analysis

2. Bass Volume Control Circuit Analysis

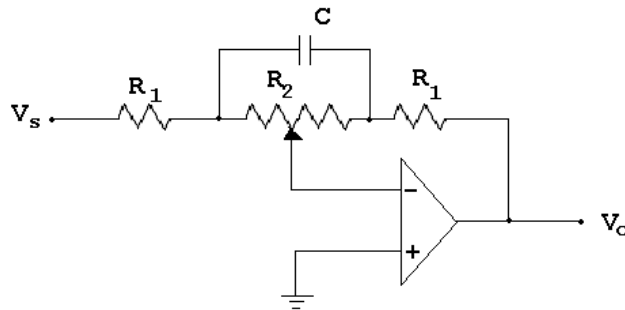- (i) Let's start from a circuit shown below.



- (ii) s-domain circuit becomes:

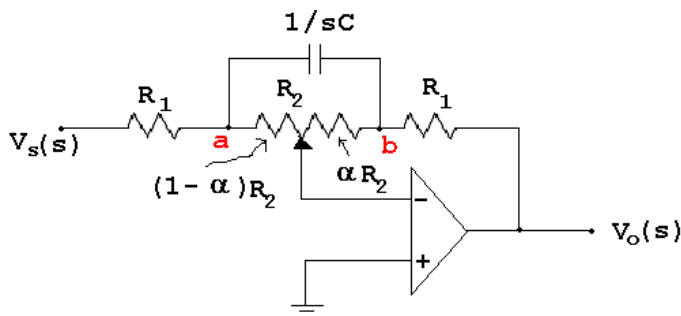

(iii) Node voltage equations:

$$\text{@node a: } \frac{V_a - V_s}{R_1} + \frac{V_a}{(1-\alpha)R_2} + \frac{V_a - V_b}{1/sC} = 0$$

$$\text{@node b: } \frac{V_b}{\alpha R_2} + \frac{V_b - V_a}{1/sC} + \frac{V_b - V_o}{R_1} = 0$$

$$\text{@center of the variable resistor: } \frac{-V_a}{(1-\alpha)R_2} + \frac{-V_b}{\alpha R_2} = 0$$

$$\text{(iv) Then, the transfer function becomes: } H(s) = \frac{V_o}{V_s} = \frac{-(R_1 + \alpha R_2 + R_1 R_2 C s)}{R_1 + (1-\alpha)R_2 + R_1 R_2 C s}$$

(v) The magnitude of steady-state transfer function is:

$$|H(j\omega)| = \frac{|(R_1 + \alpha R_2) + j\omega R_1 R_2 C|}{|(R_1 + (1-\alpha)R_2) + j\omega R_1 R_2 C|} \dots\dots(1)$$

3. Analysis of the Bass Volume Control Transfer Function

(i) Let's consider the equation (1) with different values of α .

(ii) If $\alpha=0.5$, $|H(j\omega)| = \frac{|(R_1 + 0.5R_2) + j\omega R_1 R_2 C|}{|(R_1 + 0.5R_2) + j\omega R_1 R_2 C|} = 1$. Therefore there is no

amplification or attenuation

(iii) Volume control (Amplification or Attenuation) is controlled by the values of α .

(iv) Numerical values of R_1 , R_2 , and C are determined by the following 2 design decisions

(a) Passband amplification in the Bass range ($\omega \rightarrow 0$)

(b) The frequency at which the amplification is changed by 3dB (cutoff)

4. Procedures for finding the numerical values based on the design decisions

(i) The maximum magnitude relationship (remember it is a LPF)

$$|H(j\omega)|_{\max} = |H(j0)|_{\alpha=1} = \frac{R_1 + R_2}{R_1}$$

(ii) Minimum magnitude relationship

$$|H(j\omega)|_{\min} = |H(j0)|_{\alpha=0} = \frac{R_1}{R_1 + R_2}$$

(iii) Cutoff frequency relationship (*Derivation of this follows*)

$$|H(j\omega)|_{\text{cutoff}} = \frac{1}{\sqrt{2}} |H(j\omega)|_{\max} = \frac{1}{\sqrt{2}} \frac{R_1 + R_2}{R_1}$$

$$\text{or } |H(j\omega_c)| = \frac{1}{\sqrt{2}} |H(j0)|_{\alpha=1} = \frac{1}{\sqrt{2}} \frac{R_1 + R_2}{R_1}$$

(iv) The magnitude at the cutoff frequency using equation (1):

$$|H(j\omega_c)|_{\alpha=1} = \frac{|(R_1 + R_2) + j\omega_c R_1 R_2 C|}{|(R_1 + j\omega_c R_1 R_2 C|} = \sqrt{\frac{(R_1 + R_2)^2 + (\omega_c R_1 R_2 C)^2}{R_1^2 + (\omega_c R_1 R_2 C)^2}}$$

$$\text{and it becomes: } |H(j\omega_c)|_{\alpha=1} = \sqrt{\frac{(R_1 + R_2)^2 / R_1^2 + (\omega_c R_2 C)^2}{1 + (\omega_c R_2 C)^2}}$$

(v) Let's replace ω_c by $1/R_2 C$, then the equation becomes:


$$|H(j\omega_c)|_{\alpha=1} = \sqrt{\frac{(R_1 + R_2)^2 / R_1^2 + 1}{2}}$$

(vi) To simplify the above equation, let's assume that $\frac{R_1 + R_2}{R_1} \gg 1$. Then the equation

reduces to: $|H(j\omega_c)|_{\alpha=1} = \sqrt{\frac{(R_1 + R_2)^2 / R_1^2}{2}} = \frac{1}{\sqrt{2}} \frac{R_1 + R_2}{R_1}$

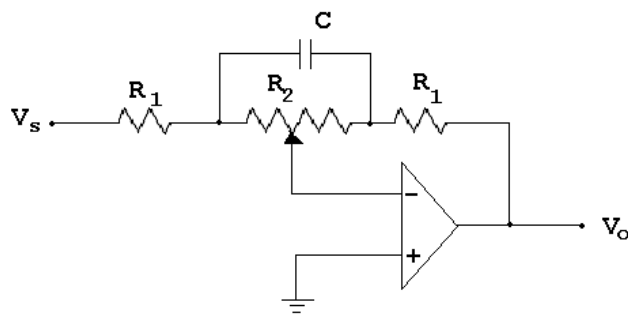5. EXAMPLE PROBLEM:

Using the circuit below, design a volume control circuit to give a maximum gain of 20dB and a gain of 17dB at a frequency of 40 Hz.



(SOLUTION)